 


CPE 233: Peripheral assignment 3, Keypad Driver

Prof. Bridget Benson

Marina Dushenko, Luis Gomez

BBD




Behavior

The **Keypad Driver** is a sequential circuit whose inputs are 1-bit signals from a 'key-press' on the keypad circuit, and whose output consists of a four 1-bit signals driving the keypad-columns, 11-bits driving a seven-segment display, and 1-bit 60ns interrupt pulse.

The Keypad Driver allows a user to interact with an external keypad circuit, reading from a 3 X 4 matrix of push-buttons. The user's button-press is registered and displayed on a seven-segment display for the duration of the key-press; releasing the button will clear the display digit.

Structural

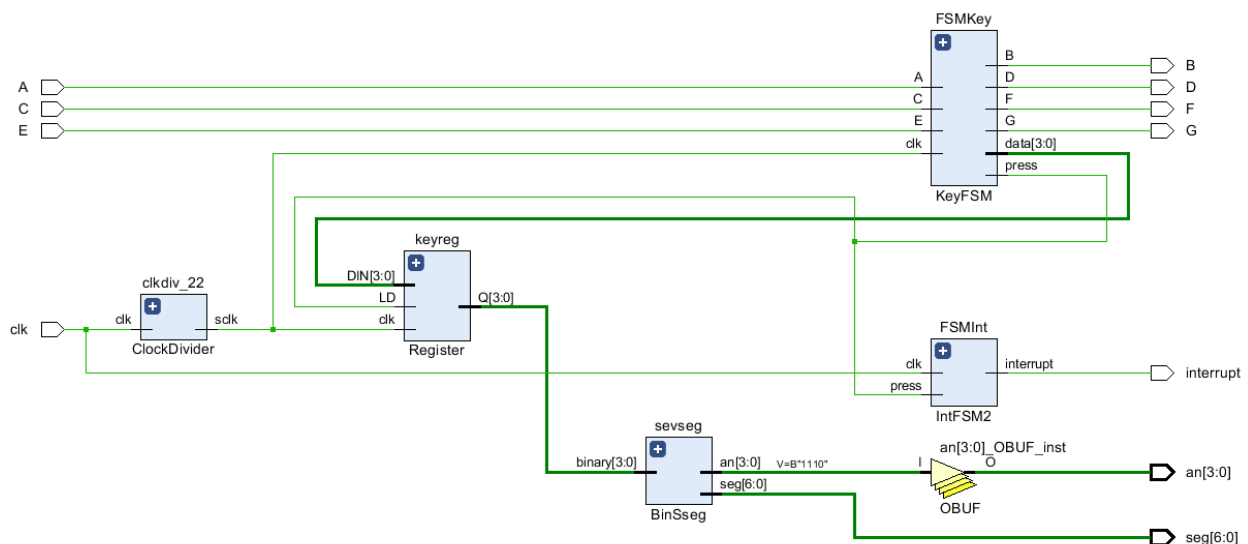The structural design of the Keypad Driver is found below:




Specifications


Operating Speed: 22Hz w/ Button Signal Debounced	Supports 3 X 4 Keypads
Input Clock: 100Mhz	Output: 3.3 V 60ns Interrupt pulse
Output Characters: 0-9, 'A', 'b' to a Seven-Segment Display	

The Key-Pad driver consists of various modules:

- **Key-Press FSM:** Finite state machine which drives high signal through a keypad column each cycle (22 hz). Four states are State B, State G, State F, State D. During each state, the FSM reads in C, A , E inputs and drives the corresponding key-value to the 4-bit Register.
- **Interrupt FSM:** Finite state machine which drives the 60ns Interrupt signal. The FSM has seven states 0-7, during each state the FSM checks if a debounced-button press has been input. When a debounced button-press is detected, the FSM drives the Interrupt signal high for that cycle (10ns). Over the span of 6 additional states, the cumulative period of the interrupt signal amounts to 60ns.
- **Seven-Segment Display Driver:** Converts a 4-bit binary input into a Seven-Segment Display Digit.
- **Clock-Divider:** Generates the 22 hz 'slow' clock
- **4-bit Register:** 4-bit register with a LD input

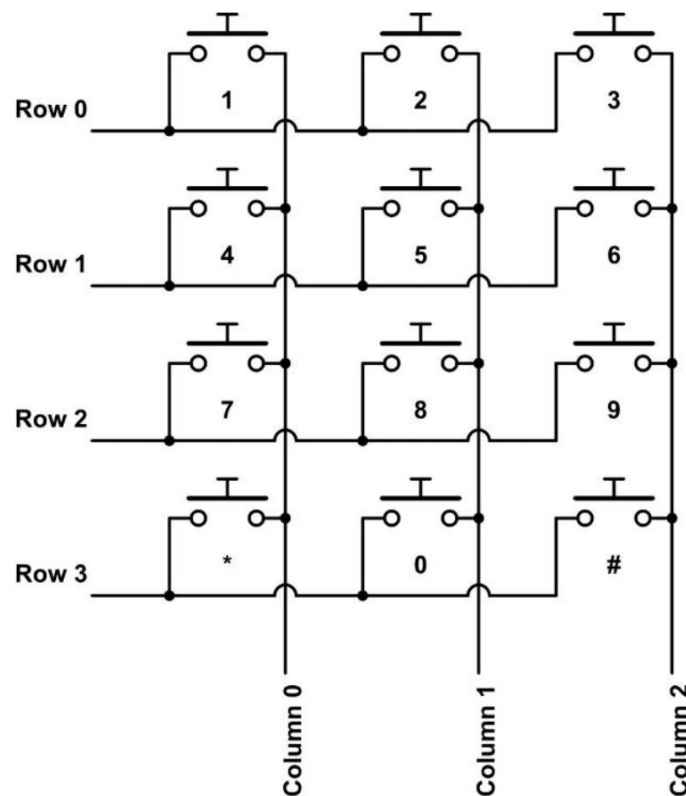

Verification

 

Interrupt Signal as seen by the Oscilloscope

Example Assembly Code

```
.EQU KEYPAD_PORT = 0x82
.CSEG
.ORG 0x1
; Code Demonstrating use of the Key Pad Driver
; 8-bit counter with LD

        SEI
start:   MOV R0, 0x00
count:   ADD R0, 0x01
        CMP R0, 0xFF
        BRNE count
        BRN start

.CSEG
.ORG 0x3FF
ISR: IN R0, KEYPAD_PORT
        RETIE
```

System Verilog Source Code

Key-Press FSM (3pgs)

```

`timescale 1ns / 1ps

module KeyFSM(input clk, C, A, E,
              output logic B, G, F, D, press,
              output logic [3:0] data
              );

    typedef enum {STATE_B, STATE_G, STATE_F, STATE_D} STATE;
    STATE NS, PS = STATE_B;

    always_ff @ (posedge clk)
    begin
        PS <= NS;
    end

    always_comb
    begin
        case(PS)
        STATE_B:
            begin
                if(C == 1)
                begin
                    data = 1;
                    press = 1;
                end
                else if(A == 1)
                begin
                    data = 2;
                    press = 1;
                end
                else if(E == 1)
                begin
                    data = 3;
                    press = 1;
                end
                else
                begin
                    data = 13;
                    press = 0;
                end
            end
        begin
            B = 1; G = 0; F = 0; D = 0;
            NS = STATE_G;
        end
    end
end

```

```
STATE_G:
begin
  if(C == 1)
    begin
      data = 4;
      press = 1;
    end
  else if(A == 1)
    begin
      data = 5;
      press = 1;
    end
  else if(E == 1)
    begin
      data = 6;
      press = 1;
    end
  else
    begin
      data = 12;
      press = 0;
    end
  begin
    B = 0; G = 1; F = 0; D = 0;
    NS = STATE_F;
  end
end
STATE_F:
begin
  if(C == 1)
    begin
      data = 7;
      press = 1;
    end
  else if(A == 1)
    begin
      data = 8;
      press = 1;
    end
  else if(E == 1)
    begin
      data = 9;
      press = 1;
    end
  else
    begin
      data = 14;
      press = 0;
    end
  begin
    B = 0; G = 0; F = 1; D = 0;
    NS = STATE_D;
  end
end
end
```

```
STATE_D:
    begin
        if(C == 1)
            begin
                data = 10;
                press = 1;
            end
        else if(A == 1)
            begin
                data = 0;
                press = 1;
            end
        else if(E == 1)
            begin
                data = 11;
                press = 1;
            end
        else
            begin
                data = 15;
                press = 0;
            end
        begin
            B = 0; G = 0; F = 0; D = 1;
            NS = STATE_B;
        end
    end
    default: NS = STATE_B;
endcase
end

endmodule
```

Interrupt FSM (2pgs)

```
`timescale 1ns / 1ps

module IntFSM2(
    input clk, press,
    output logic interrupt
);

typedef enum {ST0, ST1, ST2, ST3, ST4, ST5, ST6, ST7} STATE;
STATE NS, PS = ST0;

always_ff @ (posedge clk)
begin
    PS <= NS;
end

always_comb
begin
    interrupt = 0 ;
    case(PS)
        ST0:
            begin
                if (press == 0)
                begin
                    interrupt = 0;
                    NS = ST0;
                end
                else
                    NS = ST1;
            end
        ST1:
            begin
                if(press == 1)
                    interrupt = 1;
                    NS = ST2;
            end
        ST2:
            begin
                if(press == 1)
                    interrupt = 1;
                    NS = ST3;
            end
        ST3:
            begin
                if(press == 1)
                    interrupt = 1;
                    NS = ST4;
            end
            end
    end
end
```



```
ST4:
  begin
    if (press == 1)
      interrupt = 1;
      NS = ST5;
    end
  ST5:
    begin
      if (press == 1)
        interrupt = 1;
        NS = ST6;
      end
    ST6:
      begin
        if (press == 1)
          interrupt = 1;
          NS = ST7;
        end
      ST7:
        begin
          if (press == 1)
            begin
              interrupt = 0;
              NS = ST7;
            end
          else
            NS = ST0;
          end
        default: NS = ST0;
        endcase
      end
    endmodule
```

4-bit Register

```
module Register(input clk, LD,  
               input [3:0] DIN,  
               output logic [3:0] Q  
               );  
  
    always_ff @ (posedge clk)  
    begin  
        case(LD)  
            1: Q <= DIN;  
            0: Q <= Q;  
        endcase  
    end  
  
endmodule
```

Clock Divider

```
module ClockDivider(  
    input clk,  
    output logic sclk);  
  
    localparam MAX_COUNT = 2272727;  
    logic [26:0] count = 0;  
  
    always_ff @ (posedge clk)  
    begin  
        count <= count + 1;  
        if (count == MAX_COUNT)  
        begin  
            count <= 0;  
            sclk <= ~sclk;  
        end  
    end  
end  
endmodule
```

Seven Segment Display Driver

```
module BinSseg(
    input [3:0] binary,
    output logic [6:0] seg,
    output [3:0] an
);

//always block for converting binary into 7 segment format
always_comb
begin
    case (binary) //case statement
        0 : seg = 7'b1000000;
        1 : seg = 7'b1111001;
        2 : seg = 7'b0100100;
        3 : seg = 7'b0110000;
        4 : seg = 7'b0011001;
        5 : seg = 7'b0010010;
        6 : seg = 7'b0000010;
        7 : seg = 7'b1111000;
        8 : seg = 7'b0000000;
        9 : seg = 7'b0010000;
        10: seg = 7'b0001000;
        11: seg = 7'b0000011;
        12: seg = 7'b1000110;
        13: seg = 7'b0100001;
        14: seg = 7'b0000110;
        15: seg = 7'b1111111; // Shuts off output
        //15: seg = 7'b0001110;
        //switch off 7 segment character when the bcd digit
        is not a decimal number.
        default : seg = 7'b1111111;
    endcase
end

    assign an = 4'b1110;

endmodule
```