 


CPE 233: RAT assignment 4, ALU

Prof. Bridget Benson

Luis Gomez, Matt Bailey

BBD

**Figure 1: ALU Black Box Diagram****Behavior**


In this assignment, we built an Arithmetic Logic Unit in System Verilog. The module behavior can be described as following:

Arithmetic Logic Unit (ALU): A combinatorial circuit that supports 16 instructions for the RAT architecture computer. The instructions include arithmetic operations, bit-wise operations, and logical-shift operations. The ALU also provides carry and zero flags for use in these operations. The tables below outline the inputs, outputs, and operations provided by the module:

SEL	Instruction		SEL	Instruction
0000	ADD		1000	TEST
0001	ADDC		1001	LSL
0010	SUB		1010	LSR
0011	SUBC		1011	ROL
0100	CMP		1100	ROR
0101	AND		1101	ASR
0110	OR		1110	MOV
0111	EXOR		1111	unused

bit width	Inputs		bit width	Outputs
8	A		8	RESULT
8	B		1	Z
4	SEL		1	C
1	CIN			


Structural Design

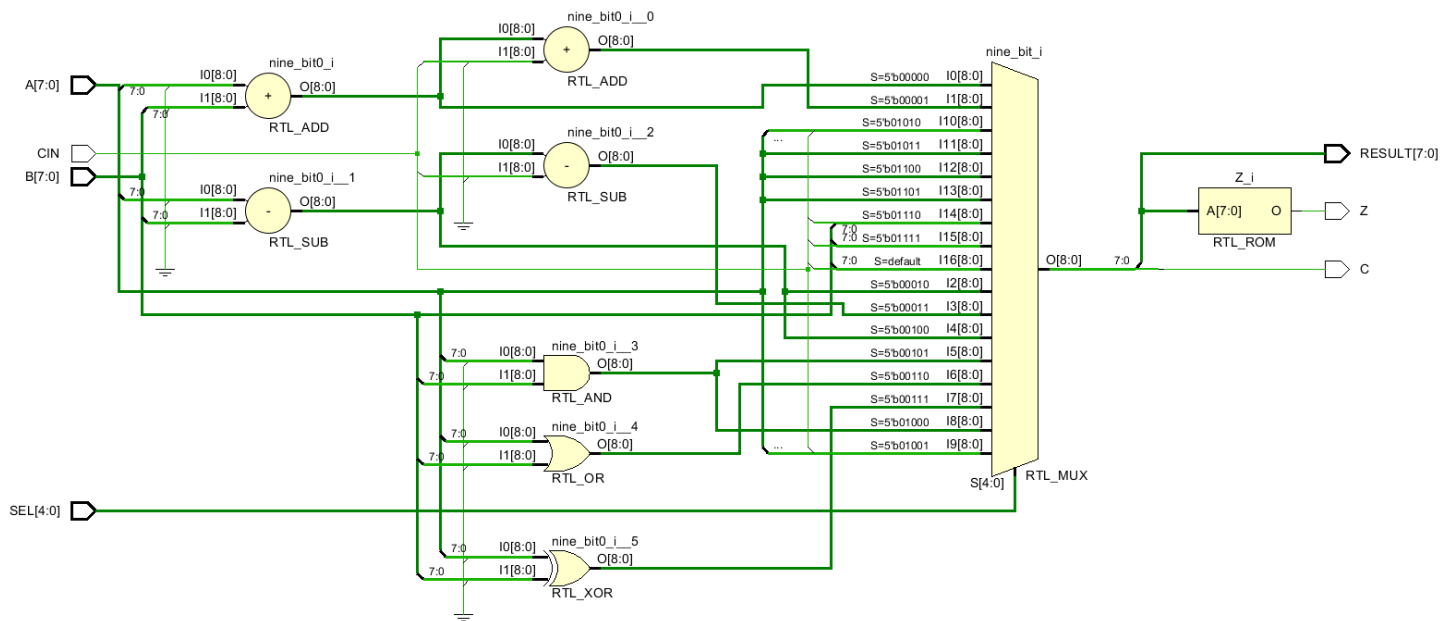

Verification


To verify the behavior of our Arithmetic Logic Unit, we created a simulation testbench that ran a total of 34 different test cases. Below we have provided a table of test case inputs, expected outputs, and testbench outputs. Further below we have provided the complete color-coded waveform, broken into three images for visual clarity. Because of the sheer number of tests, we cannot go into detail to justify the chosen parameters for each case. That said, we can generalize the description of the tests below as edge-case tests and basic functionality tests.

Waveform in its entirety

 


Waveform snippets on next page...


Waveform snippet 1: [0-10.5] ns

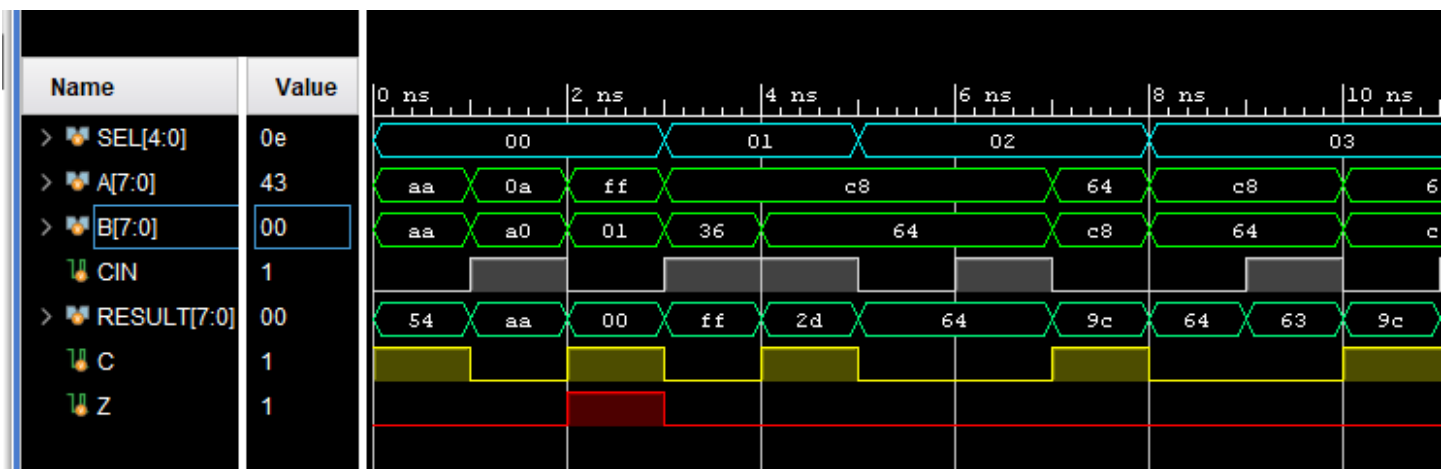

Waveform snippet 2: [10-20.5] ns

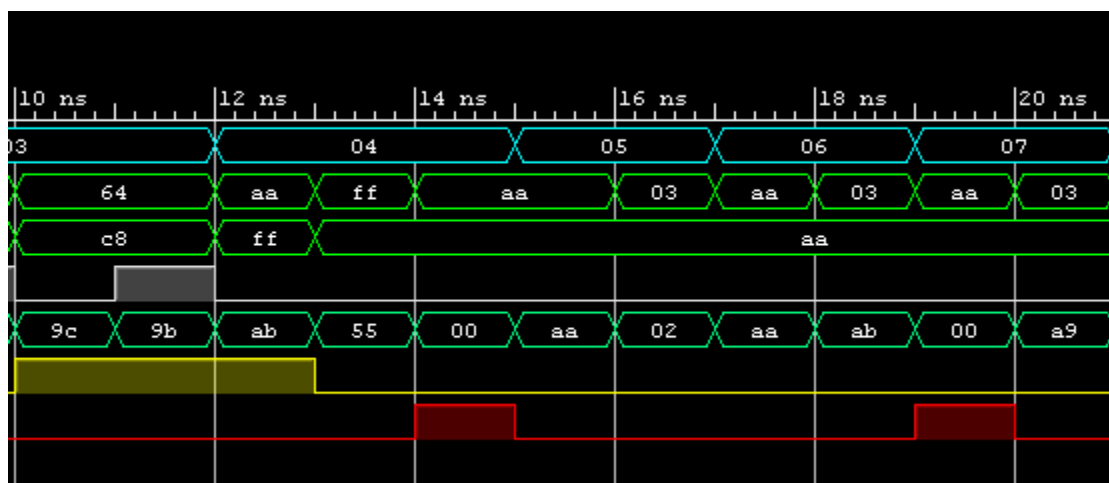

Waveform snippet 3: [20-34] ns

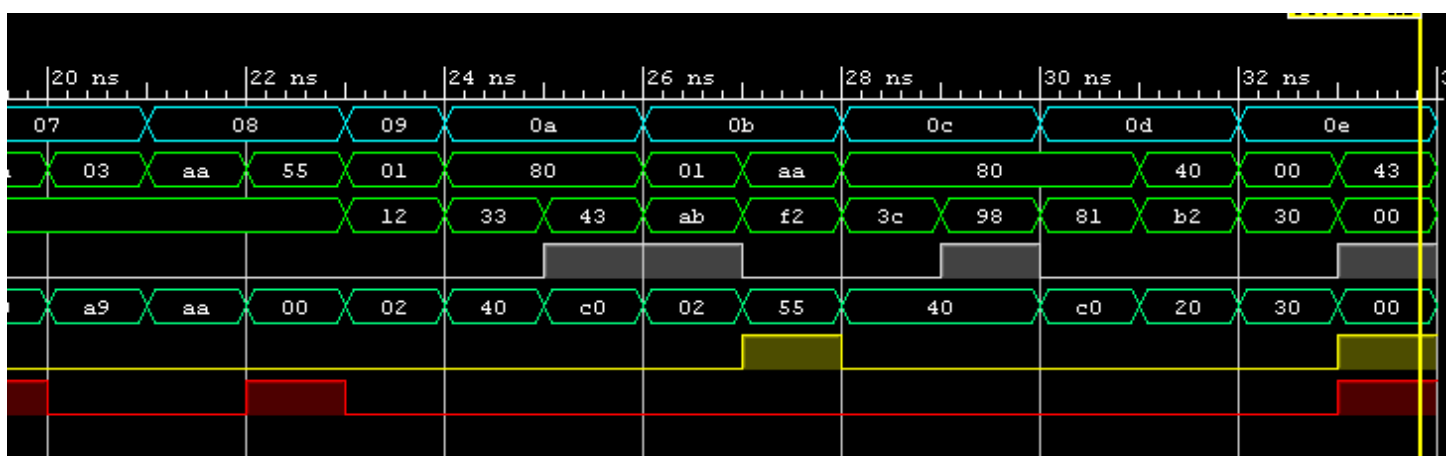

Test Cases

Test #	Function	SEL	Arguments			Expected			Testbench			Simulation Time (ns)
			A	B	Cin	Result (hex)	C	Z	Result (hex)	C	Z	
1	ADD	0000	0xAA	0xAA	0	0x54	1	0	0x54	1	0	0
2			0x0A	0xA0	1	0xAA	0	0	0xAA	0	0	1
3			0xFF	0x01	0	0x00	1	1	0x00	1	1	2
4	ADDC	0001	0xC8	0x36	1	0xFF	0	0	0xFF	0	0	3
5			0xC8	0x64	1	0x2D	1	0	0x2D	1	0	4
6	SUB	0010	0xC8	0x64	0	0x64	0	0	0x64	0	0	5
7			0xC8	0x64	1	0x64	0	0	0x64	0	0	6
8			0x64	0xC8	0	0x9C	1	0	0x9C	1	0	7
9	SUBC	0011	0xC8	0x64	0	0x64	0	0	0x64	0	0	8
10			0xC8	0x64	1	0x63	0	0	0x63	0	0	9
11			0x64	0xC8	0	0x9C	1	0	0x9C	1	0	10
12			0x64	0xC8	1	0x9B	1	0	0x9B	1	0	11
13	CMP	0100	0xAA	0xFF	0	0xAB	1	0	0xAB	1	0	12
14			0xFF	0xAA	0	0x55	0	0	0x55	0	0	13
15			0xAA	0xAA	0	0x00	0	1	0x00	0	1	14
16	AND	0101	0xAA	0xAA	0	0xAA	0	0	0xAA	0	0	15
17			0x03	0xAA	0	0x02	0	0	0x02	0	0	16
18	OR	0110	0xAA	0xAA	0	0xAA	0	0	0xAA	0	0	17
19			0x03	0xAA	0	0xAB	0	0	0xAB	0	0	18
20	EXOR	0111	0xAA	0xAA	0	0x00	0	1	0x00	0	1	19
21			0x03	0xAA	0	0xA9	0	0	0xA9	0	0	20
22	TEST	1000	0xAA	0xAA	0	0xAA	0	0	0xAA	0	0	21
23			0x55	0xAA	0	0x00	0	1	0x00	0	1	22
24	LSL	1001	0x01	0x12	0	0x02	0	0	0x02	0	0	23
25	LSR	1010	0x80	0x33	0	0x40	0	0	0x40	0	0	24
26			0x80	0x43	1	0xC0	0	0	0xC0	0	0	25
27	ROL	1011	0x01	0xAB	1	0x02	0	0	0x02	0	0	26
28			0xAA	0xF2	0	0x55	1	0	0x55	1	0	27
29	ROR	1100	0x80	0x3C	0	0x40	0	0	0x40	0	0	28
30			0x80	0x98	1	0x40	0	0	0x40	0	0	29
31	ASR	1101	0x80	0x81	0	0xC0	0	0	0xC0	0	0	30
32			0x40	0xB2	0	0x20	0	0	0x20	0	0	31
33	MOV	1110	0x00	0x30	0	0x30	0	0	0x30	0	0	32
34			0x43	0x00	1	0x00	1	1	0x00	1	1	33

TESTBENCH (3 pgs)

```
`timescale 1ns / 1ps

module ALU_tb();
    logic [4:0] SEL;           // input
    logic [7:0] A, B;         // input
    logic CIN;                // input
    logic [7:0] RESULT = 0;   // output
    logic C = 0, Z = 0;       // output

    ALU ALU_DUT(.*) ;

    initial begin // 34 Tests Total
        // Test 1:  ADD
        SEL = 0; A = 8'hAA; B = 8'hAA; CIN = 0;
        #1; // nanosecond
        // Test 2:
        SEL = 0; A = 8'h0A; B = 8'hA0; CIN = 1;
        #1;
        // Test 3:
        SEL = 0; A = 8'hFF; B = 8'h01; CIN = 0;
        #1;
        // Test 4:  ADDC
        SEL = 1; A = 8'hC8; B = 8'h36; CIN = 1;
        #1;
        // Test 5:
        SEL = 1; A = 8'hC8; B = 8'h64; CIN = 1;
        #1;
        // Test 6:  SUB
        SEL = 2; A = 8'hC8; B = 8'h64; CIN = 0;
        #1;
        // Test 7:
        SEL = 2; A = 8'hC8; B = 8'h64; CIN = 1;
        #1;
        // Test 8:
        SEL = 2; A = 8'h64; B = 8'hC8; CIN = 0;
        #1;
        // Test 9:  SUBC
        SEL = 3; A = 8'hC8; B = 8'h64; CIN = 0;
        #1;
        // Test 10:
        SEL = 3; A = 8'hC8; B = 8'h64; CIN = 1;
        #1;
        // Test 11:
        SEL = 3; A = 8'h64; B = 8'hC8; CIN = 0;
        #1;
        // Test 12:
        SEL = 3; A = 8'h64; B = 8'hC8; CIN = 1;
        #1;
    end
endmodule
```

```
// Test 13: CMP
SEL = 4; A = 8'hAA; B = 8'hFF; CIN = 0;
#1;
// Test 14:
SEL = 4; A = 8'hFF; B = 8'hAA; CIN = 0;
#1;
// Test 15:
SEL = 4; A = 8'hAA; B = 8'hAA; CIN = 0;
#1;
// Test 16: AND
SEL = 5; A = 8'hAA; B = 8'hAA; CIN = 0;
#1;
// Test 17:
SEL = 5; A = 8'h03; B = 8'hAA; CIN = 0;
#1;
// Test 18: OR
SEL = 6; A = 8'hAA; B = 8'hAA; CIN = 0;
#1;
// Test 19:
SEL = 6; A = 8'h03; B = 8'hAA; CIN = 0;
#1;
// Test 20: EXOR
SEL = 7; A = 8'hAA; B = 8'hAA; CIN = 0;
#1;
// Test 21:
SEL = 7; A = 8'h03; B = 8'hAA; CIN = 0;
#1;
// Test 22: TEST
SEL = 8; A = 8'hAA; B = 8'hAA; CIN = 0;
#1;
// Test 23:
SEL = 8; A = 8'h55; B = 8'hAA; CIN = 0;
#1;
// Test 24: LSL
SEL = 9; A = 8'h01; B = 8'h12; CIN = 0;
#1;
// Test 25: LSR
SEL = 10; A = 8'h80; B = 8'h33; CIN = 0;
#1;
// Test 26:
SEL = 10; A = 8'h80; B = 8'h43; CIN = 1;
#1;
// Test 27: ROL
SEL = 11; A = 8'h01; B = 8'hAB; CIN = 1;
#1;
// Test 28:
SEL = 11; A = 8'hAA; B = 8'hF2; CIN = 0;
#1;
```

```
// Test 29: ROR
SEL = 12; A = 8'h80; B = 8'h3C; CIN = 0;
#1
// Test 30:
SEL = 12; A = 8'h80; B = 8'h98; CIN = 1;
#1
// Test 31: ASR
SEL = 13; A = 8'h80; B = 8'h81; CIN = 0;
#1
// Test 32:
SEL = 13; A = 8'h40; B = 8'hB2; CIN = 0;
#1
// Test 33: MOV
SEL = 14; A = 8'h00; B = 8'h30; CIN = 0;
#1
// Test 34:
SEL = 14; A = 8'h43; B = 8'h00; CIN = 1;
#1
$finish;

end
endmodule
```

Source Code

ALU

```

`timescale 1ns / 1ps

module ALU(
    input [4:0] SEL,
    input [7:0] A, B,
    input CIN,
    output logic [7:0] RESULT,
    output logic C, Z
);
    logic [8:0] nine_bit;

    always_comb
    begin
        case (SEL)
            0: nine_bit = {1'b0,A} + {1'b0,B}; // ADD
            1: nine_bit = {1'b0,A} + {1'b0,B} + {8'b0,CIN}; // ADDC
            2: nine_bit = {1'b0,A} - {1'b0,B}; // SUB
            3: nine_bit = {1'b0,A} - {1'b0,B} - {8'b0,CIN}; // SUBC
            4: nine_bit = {1'b0,A} - {1'b0,B}; // CMP
            5: nine_bit = {1'b0,A} & {1'b0,B}; // AND
            6: nine_bit = {1'b0,A} | {1'b0,B}; // OR
            7: nine_bit = {1'b0,A} ^ {1'b0,B}; // EXOR
            8: nine_bit = {1'b0,A} & {1'b0,B}; // TEST
            9: nine_bit = {A[7:0], CIN}; // LSL
            10: nine_bit = {A[0], CIN, A[7:1]}; // LSR
            11: nine_bit = {A[7], A[6:0], A[7]}; // ROL
            12: nine_bit = {A[0], A[0], A[7:1]}; // ROR
            13: nine_bit = {A[0], A[7], A[7:1]}; // ASR
            14: nine_bit = {CIN, B[7:0]}; // MOV
            15: nine_bit = {CIN, B[7:0]}; // MOV
        default: nine_bit = {CIN, B[7:0]}; // MOV
        endcase
    end

    always_comb
    begin
        C = nine_bit[8];
    end

    always_comb
    begin
        if(nine_bit[7:0] == 0)
            Z = 1;
        else Z = 0;
    end

    always_comb
    begin
        RESULT = nine_bit[7:0];
    end
endmodule

```